


Project 2


Half Adder

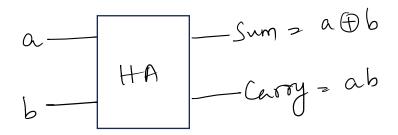

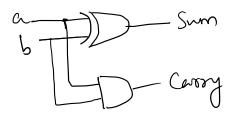


Full Adder

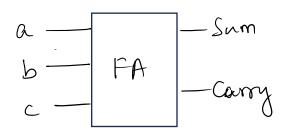

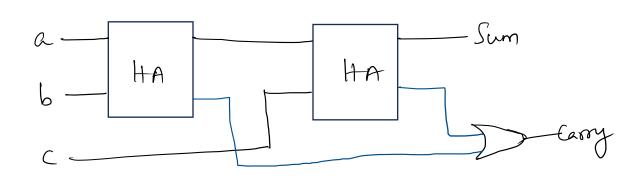


Add16 (16 bit Adder)

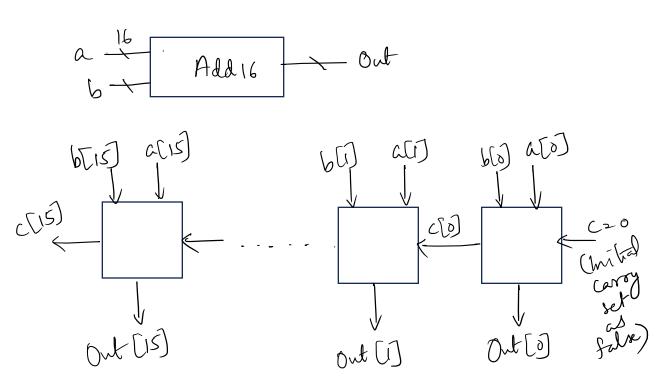

Inc16



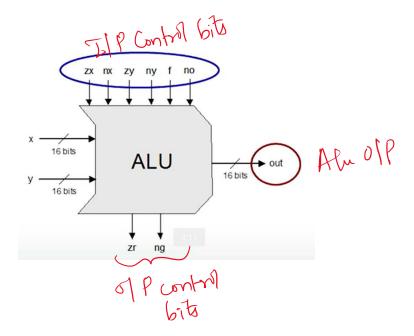

| zx | nx | zy | ny | f | no | out |
|----|----|----|----|---|----|-----|
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | -1 |
| 0 | 0 | 1 | 1 | 0 | 0 | X |
| 1 | 1 | 0 | 0 | 0 | 0 | у |
| 0 | 0 | 1 | 1 | 0 | 1 | !x |
| 1 | 1 | 0 | 0 | 0 | 1 | !y |
| 0 | 0 | 1 | 1 | 1 | 1 | -X |
| 1 | 1 | 0 | 0 | 1 | 1 | -у |
| 0 | 1 | 1 | 1 | 1 | 1 | x+1 |
| 1 | 1 | 0 | 1 | 1 | 1 | y+1 |
| 0 | 0 | 1 | 1 | 1 | 0 | x-1 |
| 1 | 1 | 0 | 0 | 1 | 0 | y-1 |
| 0 | 0 | 0 | 0 | 1 | 0 | x+y |
| 0 | 1 | 0 | 0 | 1 | 1 | х-у |
| 0 | 0 | 0 | 1 | 1 | 1 | y-x |
| 0 | 0 | 0 | 0 | 0 | 0 | x&y |
| 0 | 1 | 0 | 1 | 0 | 1 | x y |

Number of operations supported = 18

Shown in the table.

Multiplication and Division will be implemented using software later.


Note: All the operations are done in 2's complement form.

The Hack ALU operation

| pre-setting | | pre-setting | | selecting between | post-setting | Resulting |
|-------------|-------|-------------|-------|-------------------|--------------|------------|
| the x input | | the y input | | computing + or & | the output | ALU output |
| ZX | nx | zy | ny | f | no | out |
| if zx | if nx | if zy | if ny | if f | if no | out(x,y)= |
| then | then | then | then | then out=x+y | then | |
| x=0 | x=!x | y=0 | y=!y | else out=x&y | out=!out | |

| pre-setting the x input | | pre-setting the y input | | selecting between computing + or & | post-setting the output | Resulting ALU output |
|----------------------------|-----------------------|----------------------------|-----------------------|--------------------------------------|----------------------------|-------------------------|
| zx | nx | zy | ny | f | no | out |
| if zx then x=0 | if nx then x=!x | if zy then y=0 | if ny then y=!y | if f then out=x+y else out=x&y | if no then out=!out | out(x,y)= |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | -1 |
| 0 | 0 | 1 | 1 | 0 | 0 | x |
| 1 | 1 | 0 | 0 | 0 | 0 | у |
| 0 | 0 | 1 | 1 | 0 | 1 | !x |
| 1 | 1 | 0 | 0 | 0 | 1 | !y |
| 0 | 0 | 1 | 1 | 1 | 1 | -x |
| 1 | 1 | 0 | 0 | 1 | 1 | -у |
| 0 | 1 | 1 | 1 | 1 | 1 | x+1 |
| 1 | 1 | 0 | 1 | 1 | 1 | y+1 |
| 0 | 0 | 1 | 1 | 1 | 0 | x-1 |
| 1 | 1 | 0 | 0 | 1 | 0 | y-1 |
| 0 | 0 | 0 | 0 | 1 | 0 | x+y |
| 0 | 1 | 0 | 0 | 1 | 1 | x-y |
| 0 | 0 | 0 | 1 | 1 | 1 | y-x |
| 0 | 0 | 0 | 0 | 0 | 0 | x&y |
| 0 | 1 | 0 | 1 | 0 | 1 | x y |

The Hack ALU output control bits

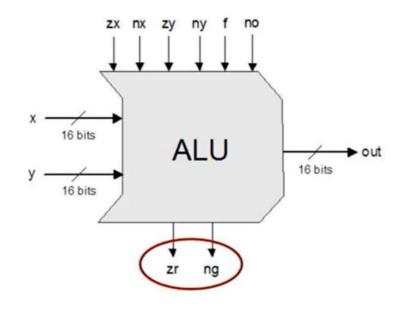

The logic can be easily deduced from the Hack Operation table.

Inputs: x,y,zx,nx,zy,ny,f,no

Outputs: Out, zr,ng

Out=0 >> zr = 1: For this we "or" all the outputs to check if out=0. If out=0 we set zr=1.

For negative numbers MSB=1. So if MSB is one implies ng=1 else ng =0. So Out[MSB] = ng

