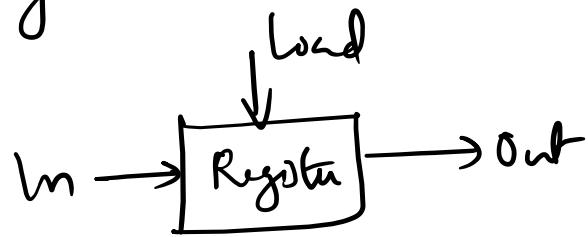


# Week 3 – Sequential Logic

Here D flipflop is given.

① 1-bit Register




If  $\text{load}[t] = 1 \Rightarrow \text{out}[t+1] = \text{in}[t]$


To read probe out. Out shows the value.

✗ Load has 2 possibilities

Load	$Q_{n+1}$
0	Out
1	in

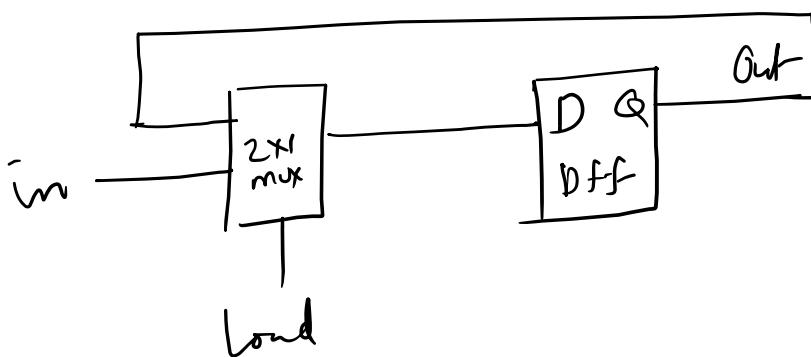

② 16 bit Register

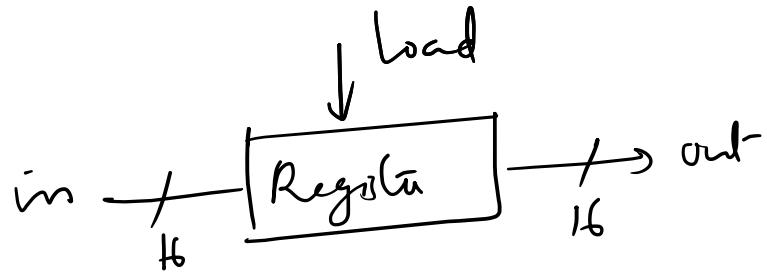


To read: probe out (out shows the value)

Write: Set in = ✓ (eg)

Set load = 1

Then on next cycle output becomes ✓

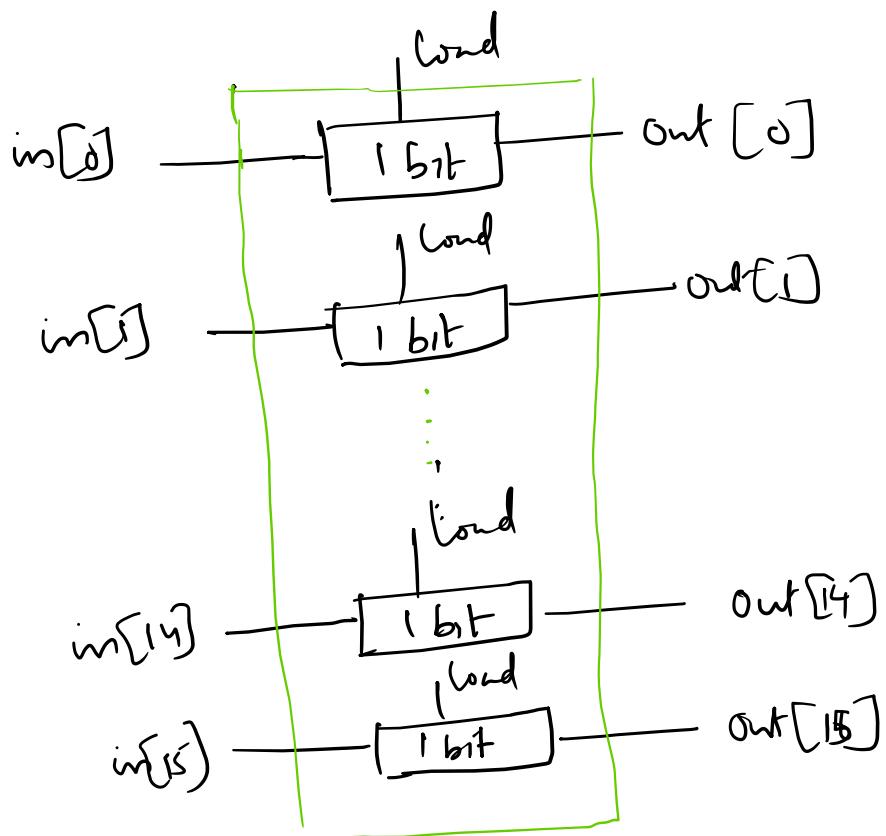


### ③ RAM8 (RAM with 8 Registers)

Given : in [16], address , load

To access 8 registers we need 3 bit address.

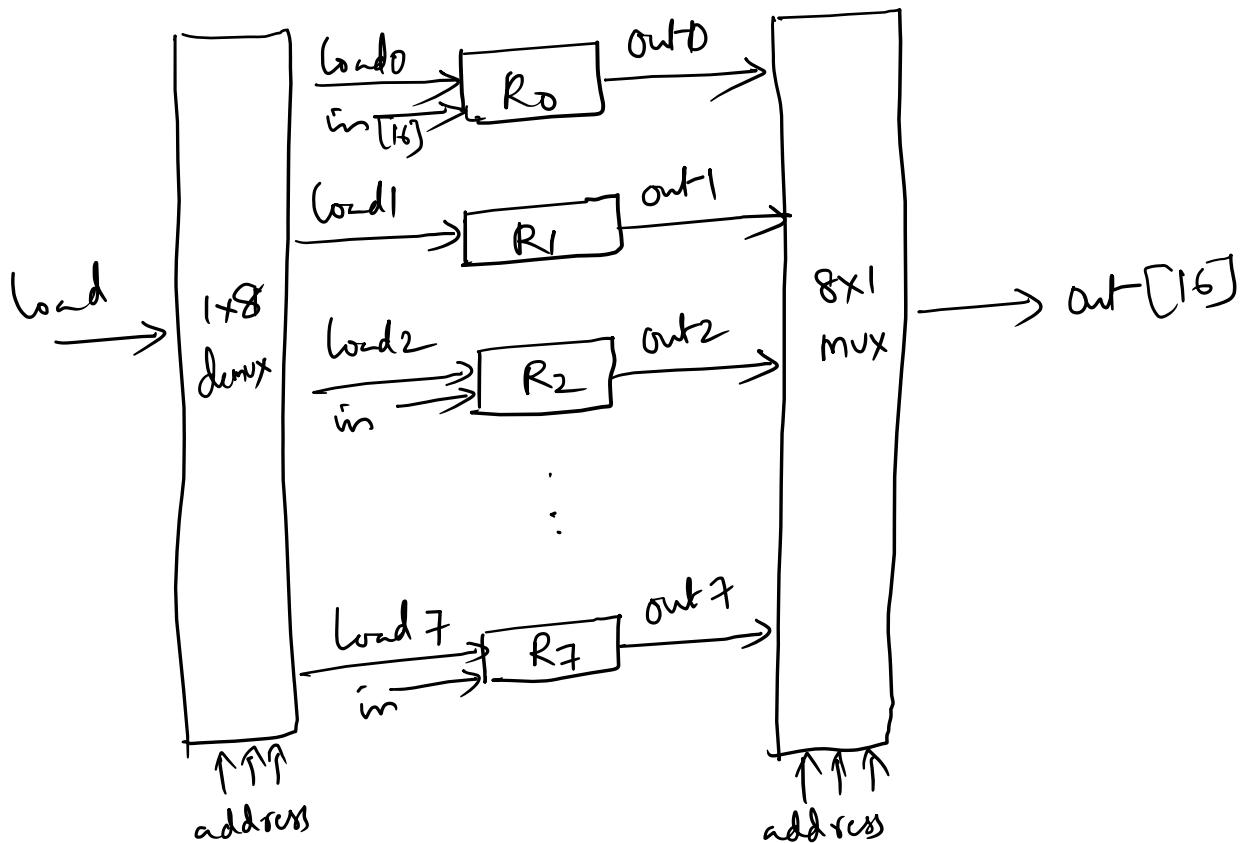
Once the register is selected , we proceed as in ② . To take output we used the same 3 bit address and select the required register .


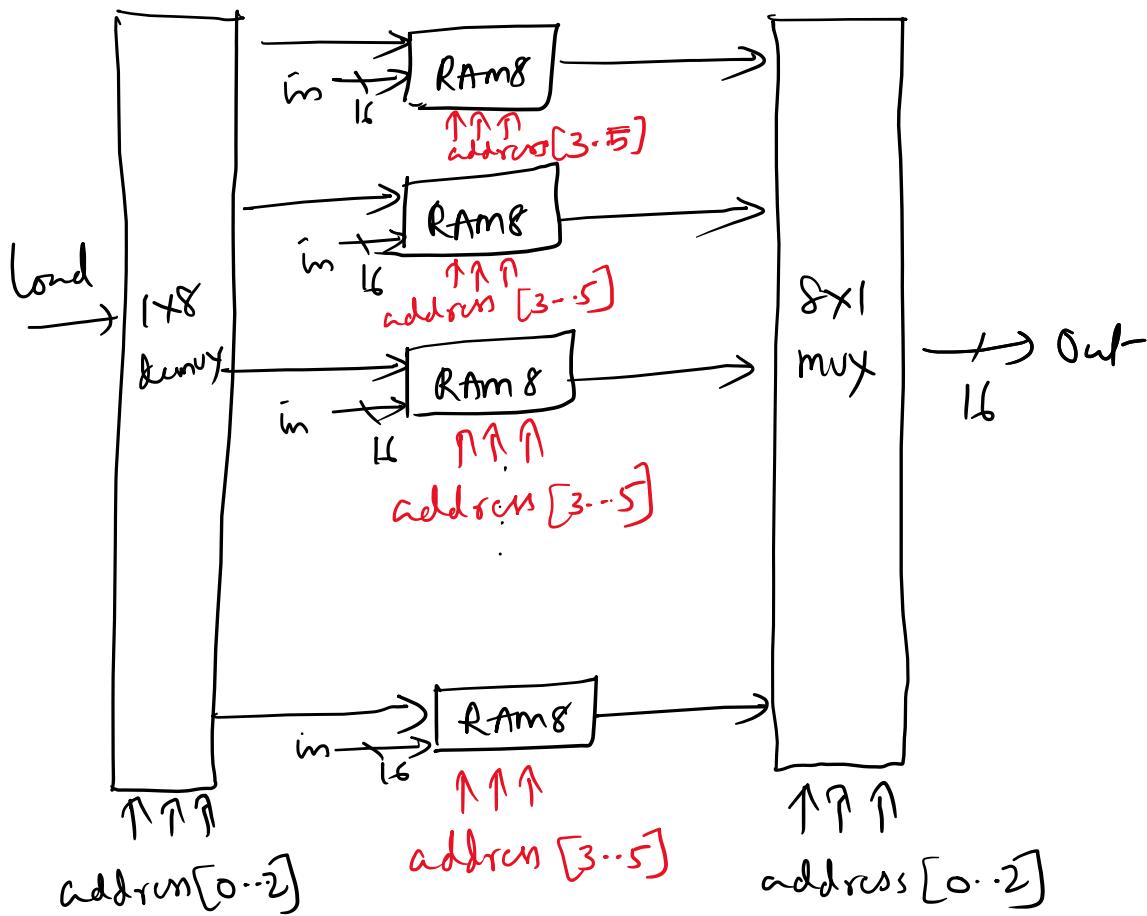
## ④ RAM64

$$\frac{64}{8} = 8 \Rightarrow 8 \text{ RAM8 can be used.}$$


To select 8 RAM stacks we need 3 bit address. Then we use 3 bit address to access the specific register as in ③.



e.g.: address  $\rightarrow$  000 001  
 Select stack 1      Select R


## ⑤ RAM 512

$$\frac{512}{64} = \frac{2^9}{2^6} = 8$$

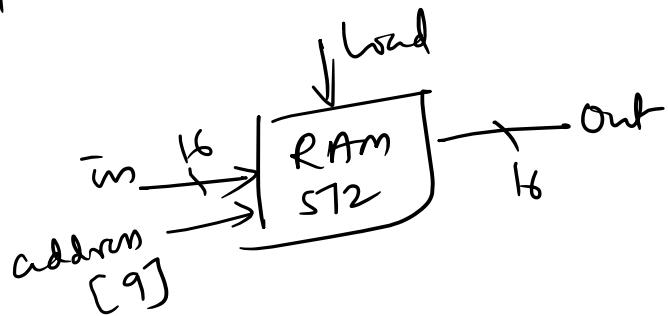

8 stacks of RAM 64 required.


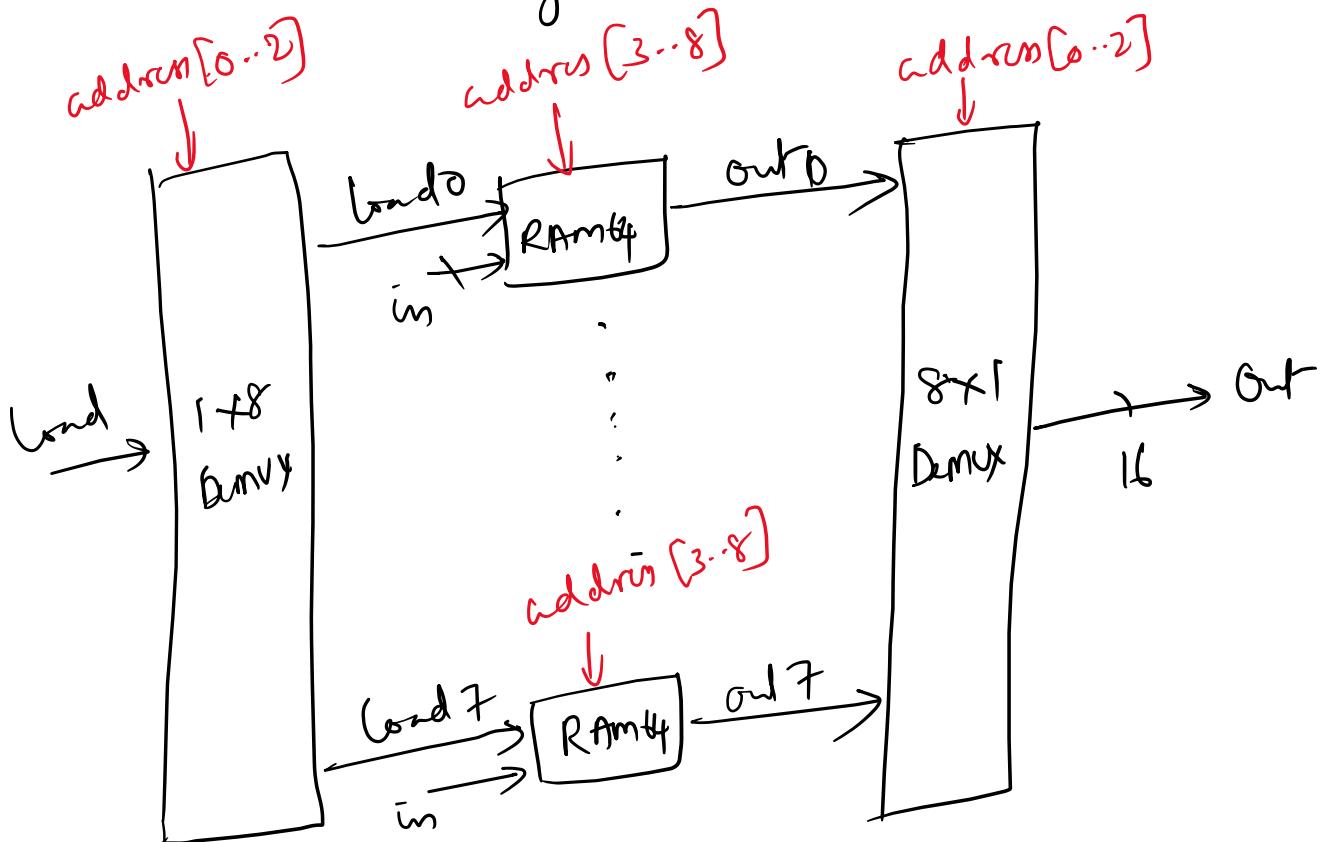
$\Rightarrow 2^3$ , i.e. 3 bit address for selecting stack  
 $64 = 2^6$ , i.e. 6 bit address for selecting the  
 Register in 64 RAM.



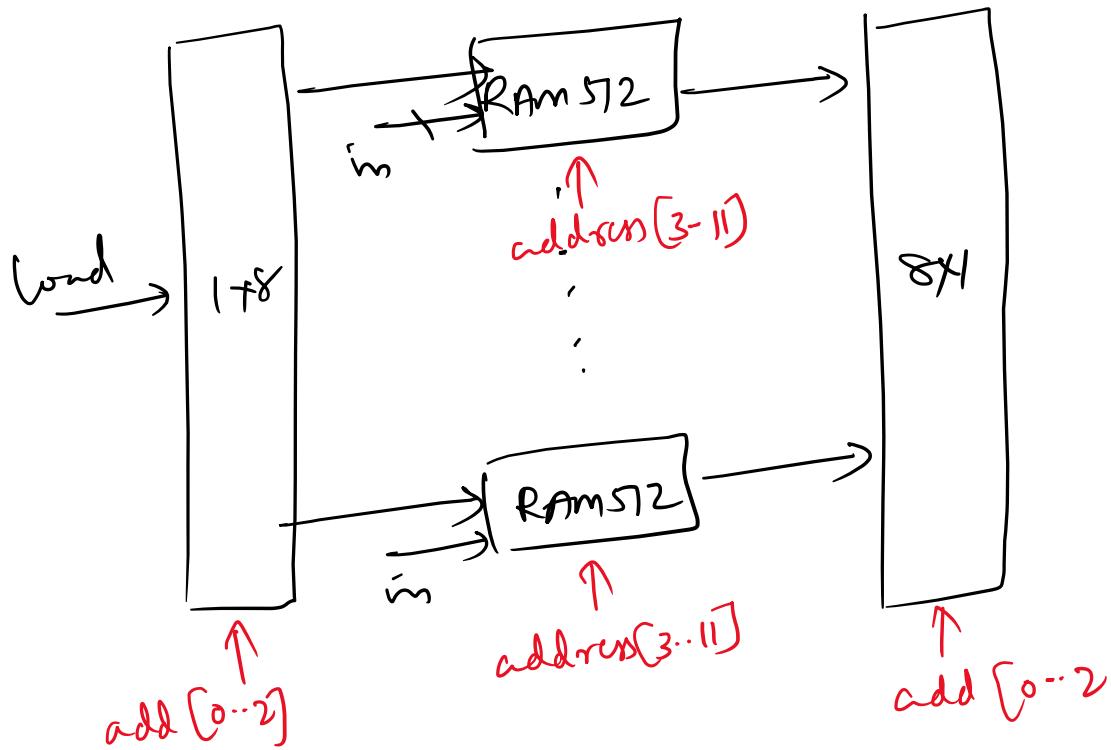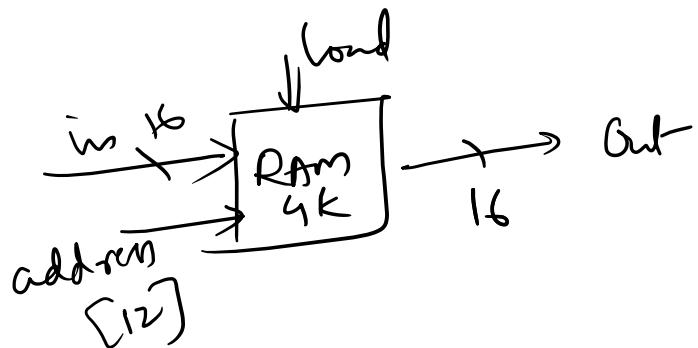
## ⑥ RAM 4K

$$\frac{4K}{572} \rightarrow \frac{4 \times 1024}{572} = 8$$


8 stacks  $\rightarrow 2^3 \rightarrow$  3 bit address  
 $572 \rightarrow 2^9 \rightarrow$  9 bit address




④ RAM 16k

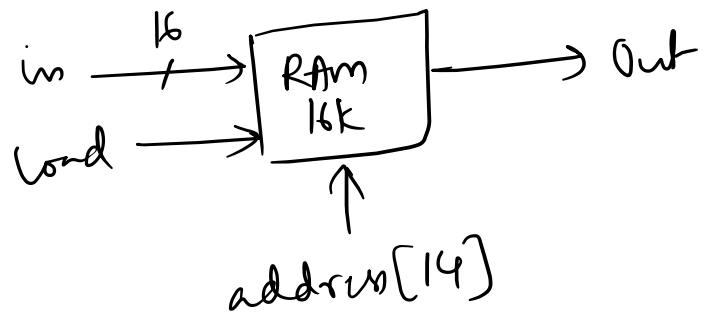
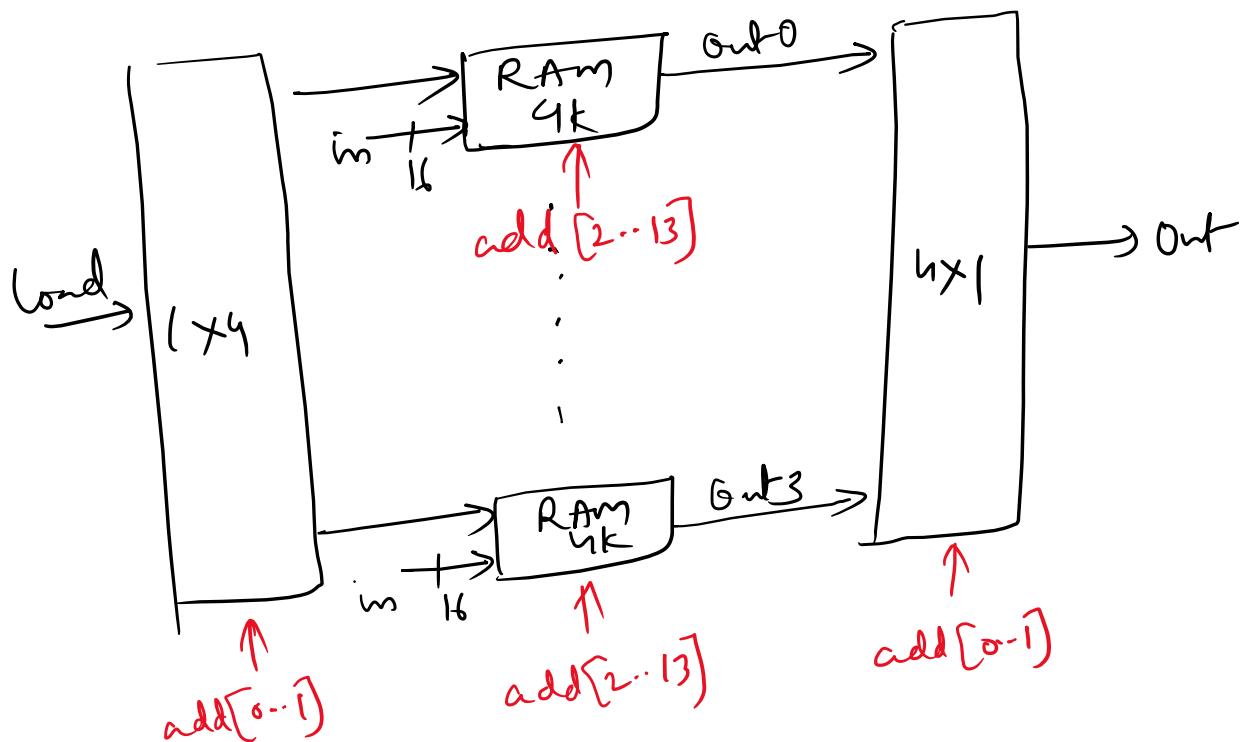
$$\frac{16K}{4K} = 4 \quad \Rightarrow \text{4 stacks (2-bit address)} \\ \Rightarrow 4K \text{ (12-bit address)}$$



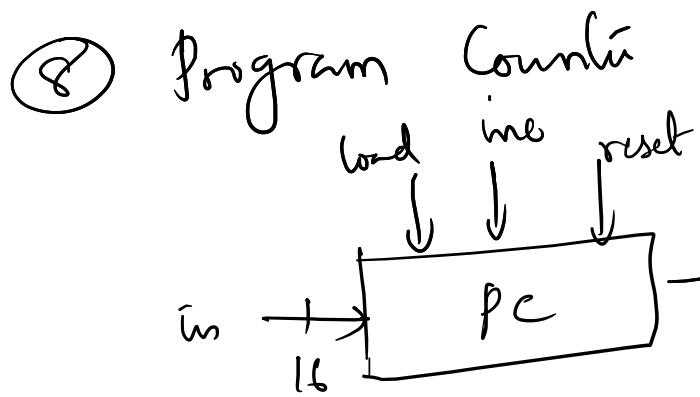


If  $\text{reset}[t-1] \Rightarrow \text{out}[t] = 0$   
 else if  $\text{load}[t-1] \Rightarrow \text{out}[t] = \text{in}[t-1]$   
 else if  $\text{inc}[t-1]$  then  $\text{out}[t] =$   
 $\text{out}[t-1] + 1$   
 else  $\text{out}[t] = \text{out}(t-1)$

$\Rightarrow$  Priority order : Reset > Load > increment


⑨ So we need a unit to do integer addition.  
 We can used inc16 from project 2.

I/Ps :  $\text{Out}[t-1]$        $\xrightarrow{\text{f/b}} \boxed{\text{inc16}}$   $\xrightarrow{\text{incout}}$   
 S/P : incout


⑩ Check reset

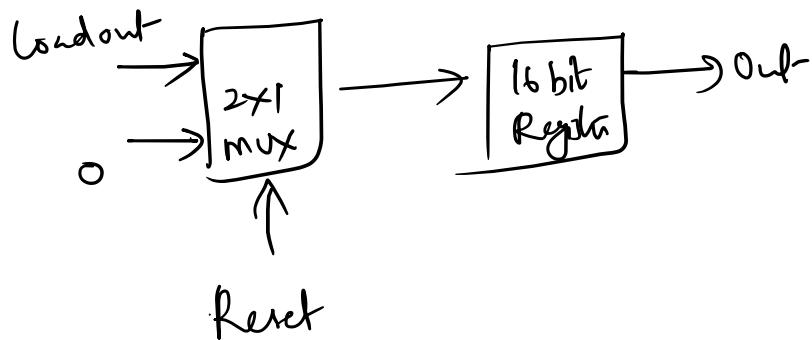

③ Check load

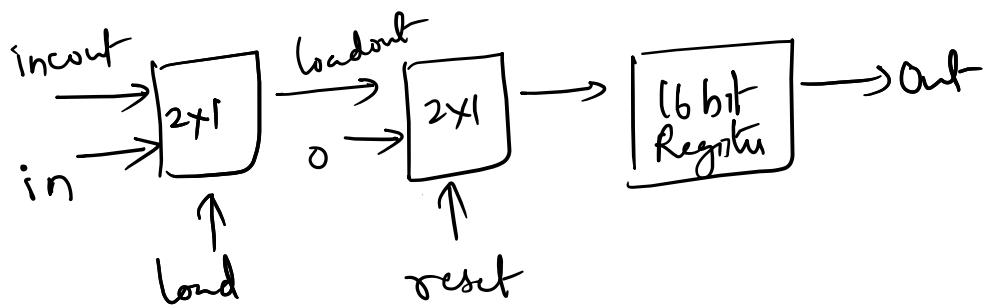

④ Check inc.

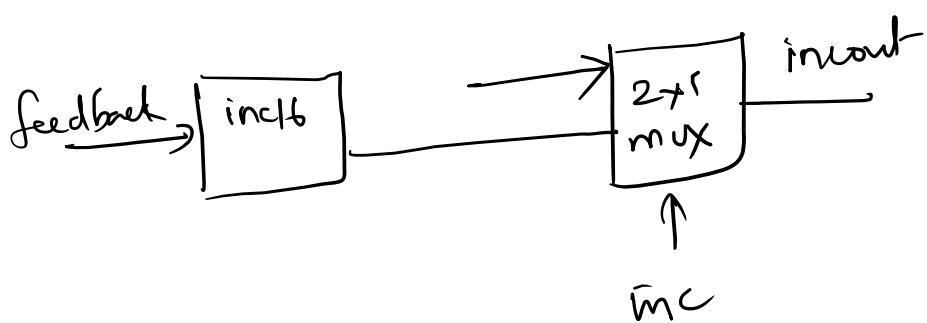

⑤ Connect together

